
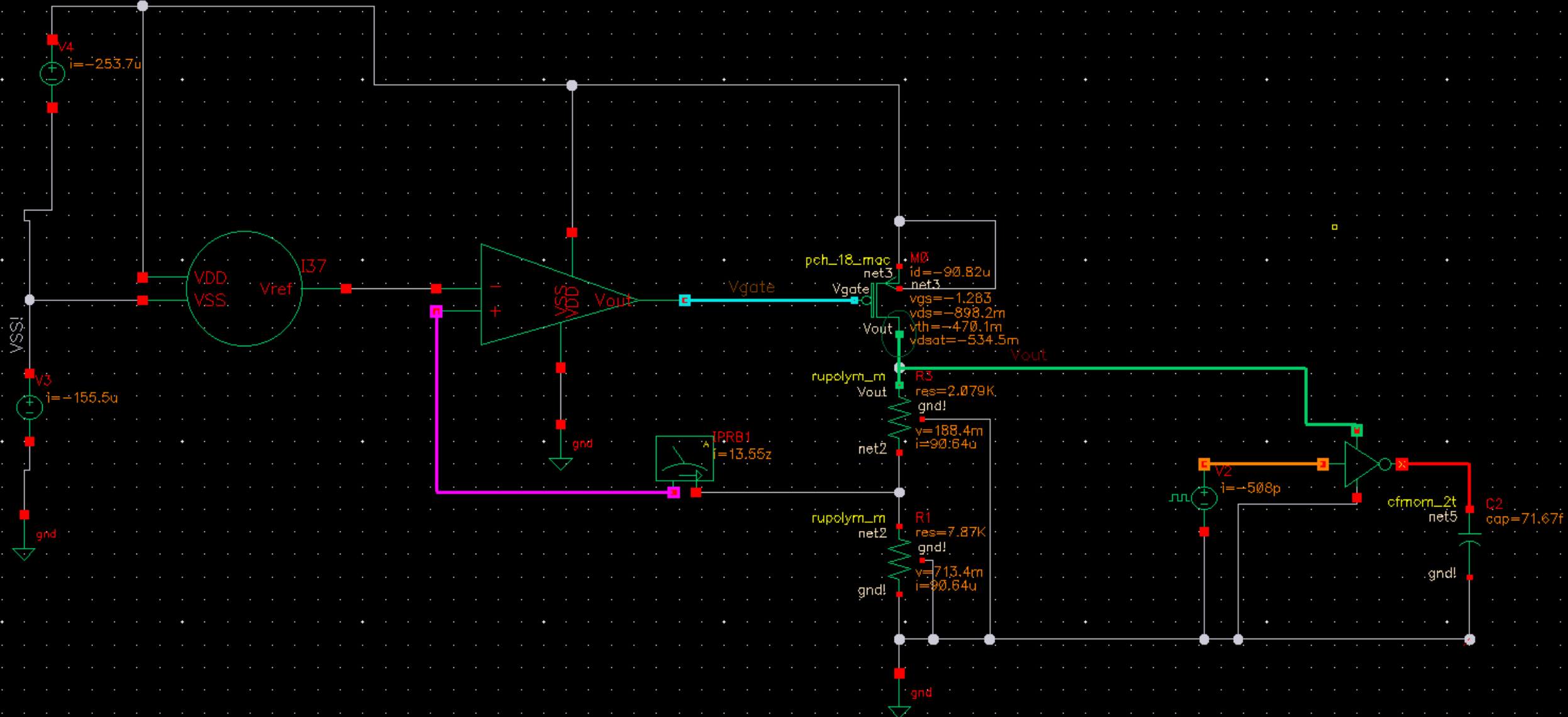


LDO

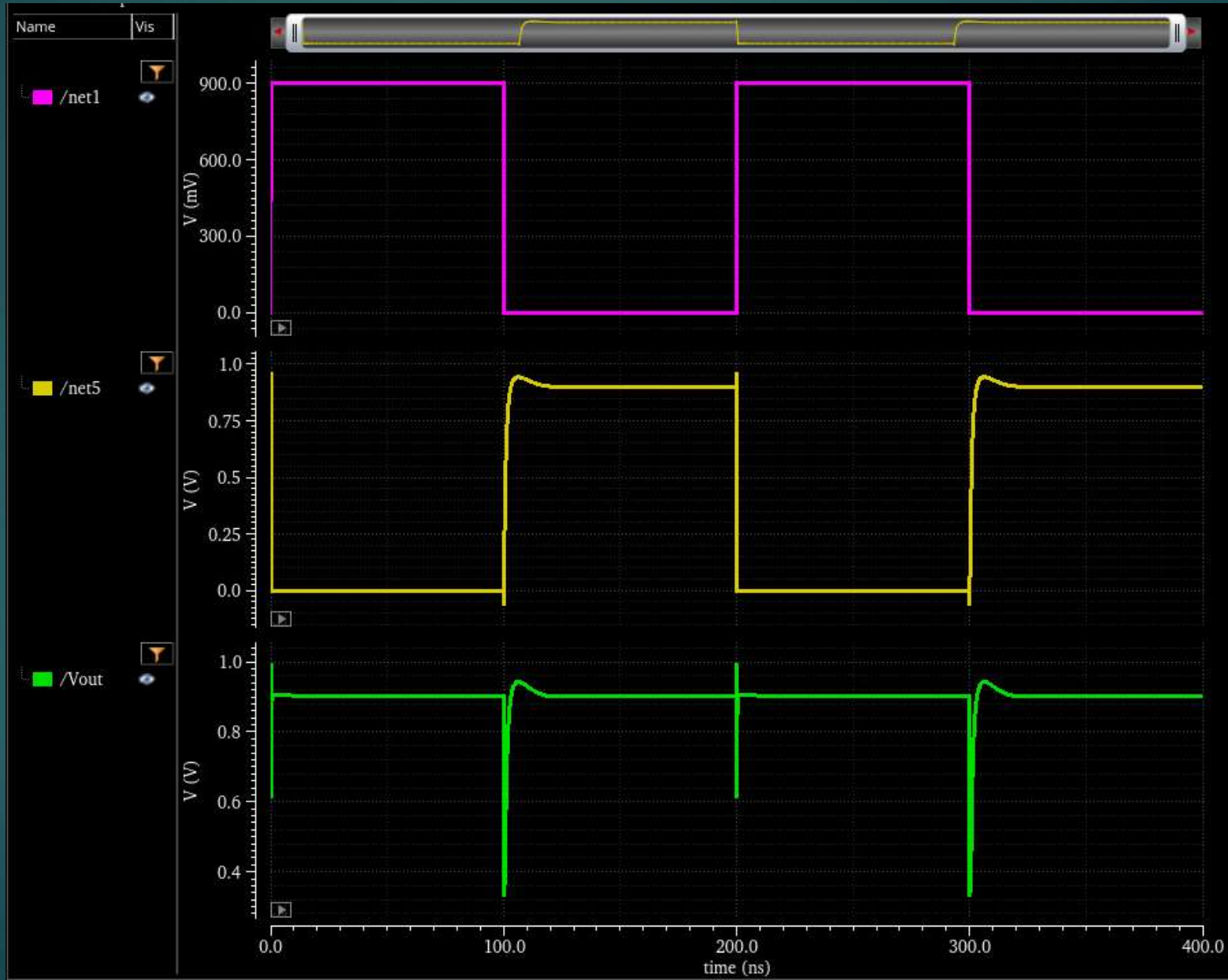


LDO – Transient Response




LDO – Frequency Response

Phase Margin = 71.37 (Deg) @ freq = 22.34M (Hz)

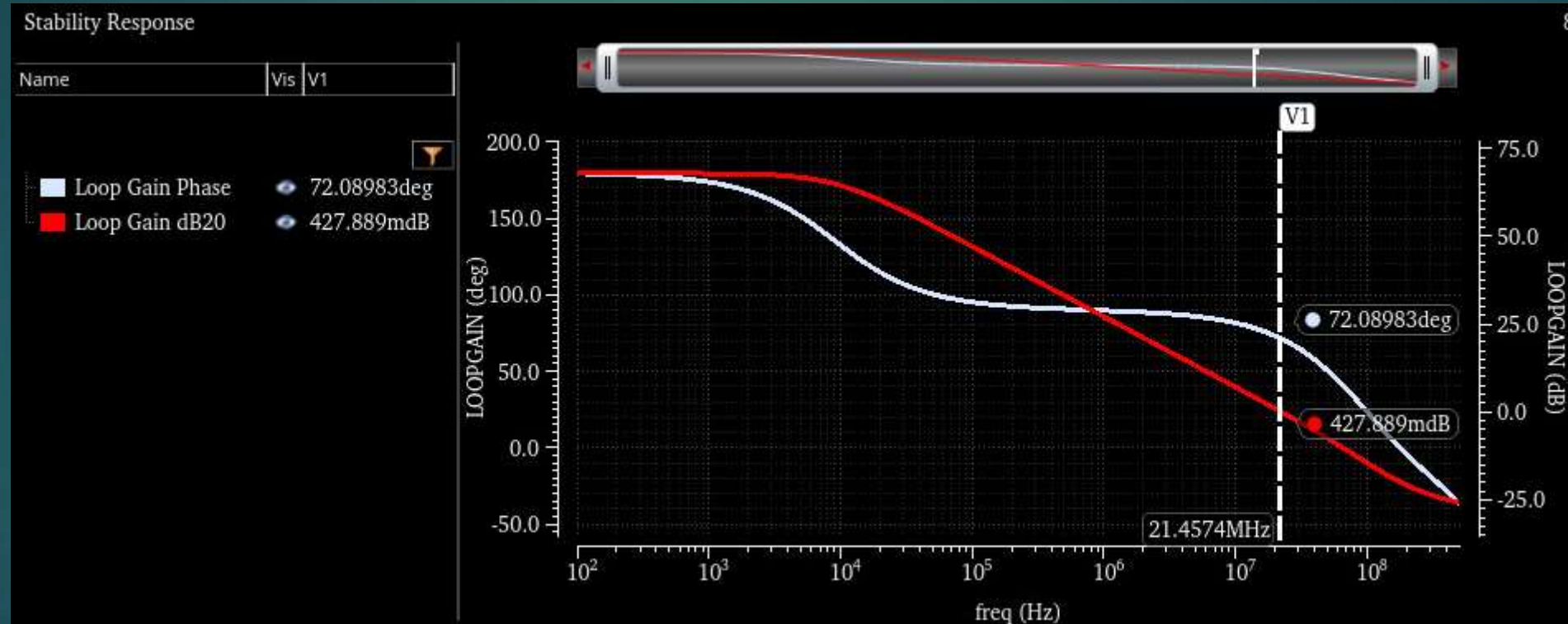Gain Margin = 19.9 (dB) @ freq = 177.8M (Hz)



- 
- What is the maximum switching frequency? In GHz?
 - What should be the average current of the LDO? What is the maximal current?

OTA

Started working on the layout of the OTA.

Currently trying to abut all transistors, still encountering some difficulties in matching their widths.

Objective now is to complete OTA & BGR layouts until mid-late Feb.

