
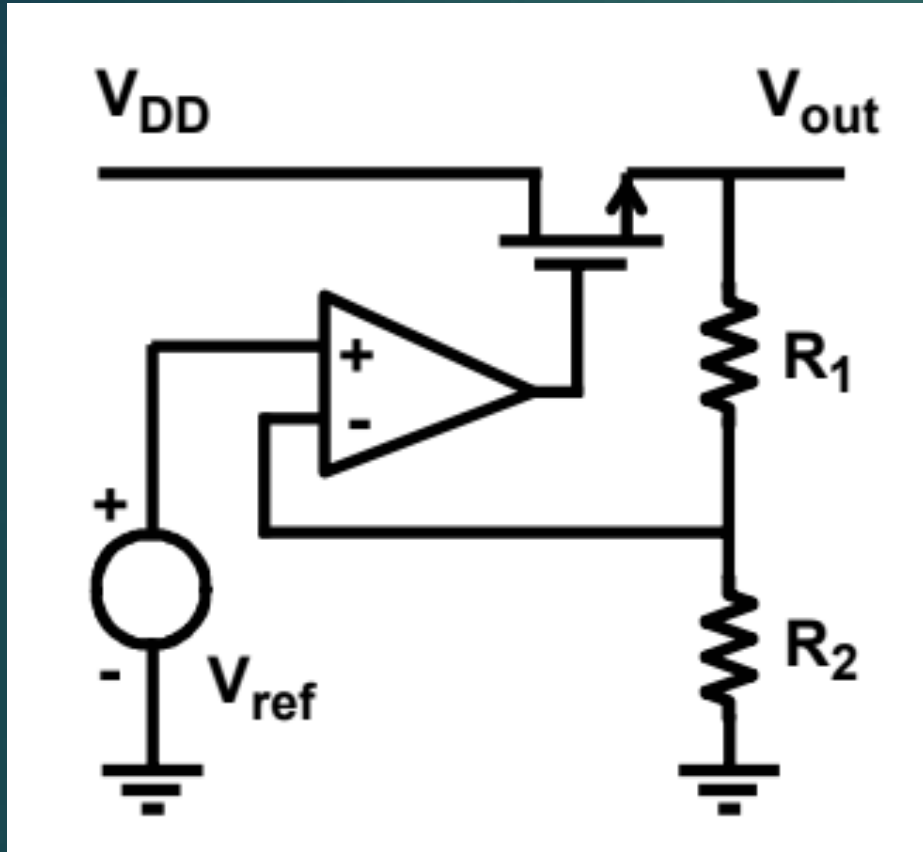



# LDO

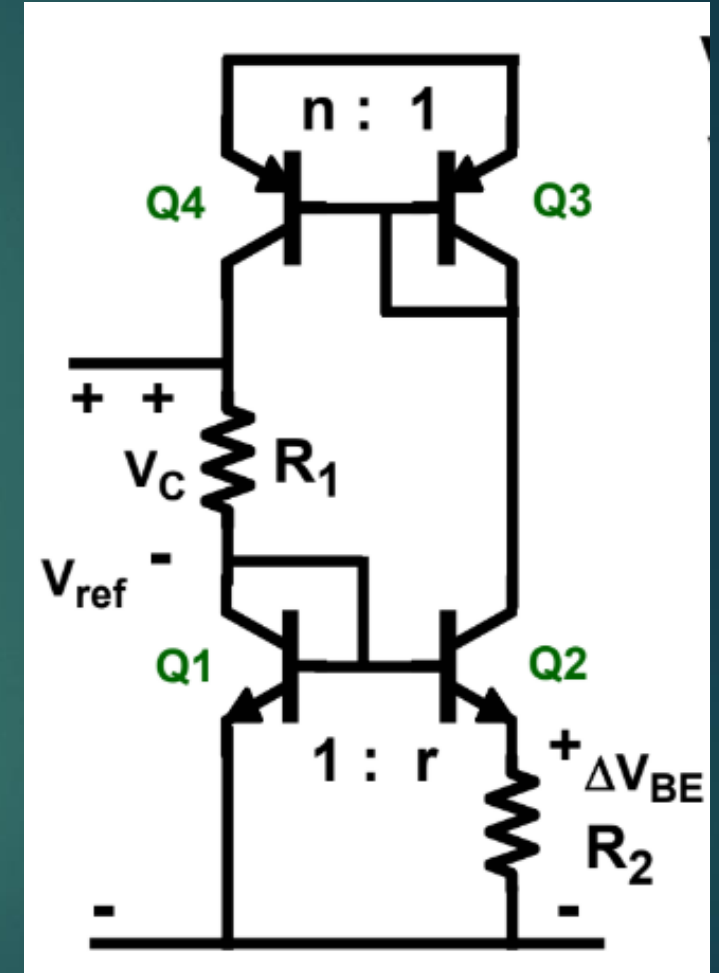

# Bandgap Reference



# LDO – Low Dropout Voltage Regulator

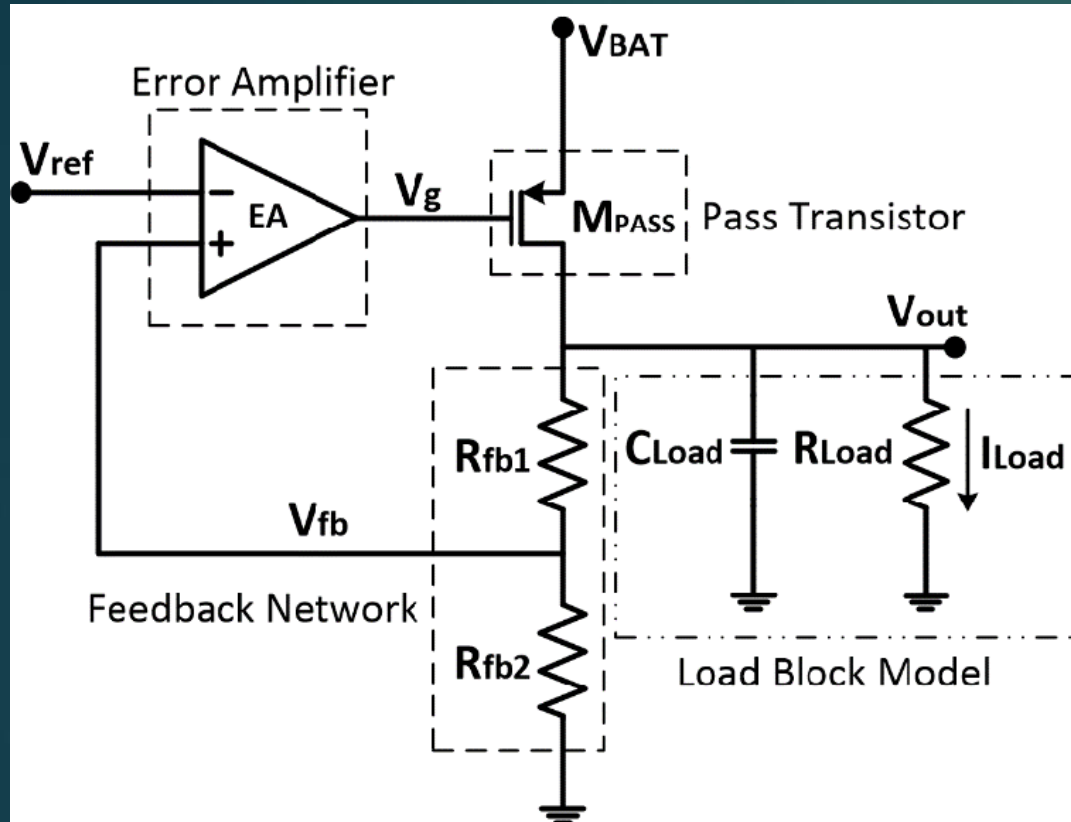

- Low dropout indicates that it can regulate  $V_{out}$  with a very small difference (dropout) between  $V_{DD}$  and  $V_{out}$ . Typically, 50-200mV.
- Regulator indicates it stabilizes the voltage and maintains it constant across a range of supply voltage and load fluctuations.
- $V_{ref}$  is given by the bandgap reference circuit and is stable across a wide temperature range: -40 to 125 degrees.
- The circuit consists of:
  - PMOS pass transistor in SAT mode – gate voltage sets current through the feedback network and the load
  - Feedback network – two resistors that form a voltage divider.
  - Op amp – compares feedback system with the ref voltage and generates the error signal to control the output voltage.

$$V_{fb} = V_{ref} = V_{out} \frac{R_{fb2}}{R_{fb1} + R_{fb2}}$$


$$V_{out} = V_{ref} \frac{R_{fb1} + R_{fb2}}{R_{fb2}}$$

If  $V_{fb} > V_{ref} \rightarrow V_g \uparrow \rightarrow V_{sg} \downarrow \rightarrow I_{SD} \downarrow \rightarrow V_{fb} \downarrow$


If  $V_{fb} < V_{ref} \rightarrow V_g \downarrow \rightarrow V_{sg} \uparrow \rightarrow I_{SD} \uparrow \rightarrow V_{fb} \uparrow$

$$I_{SD} = k(V_{GS} - V_t)^2(1 + \lambda V_{SD})$$

# Bandgap Reference Circuit

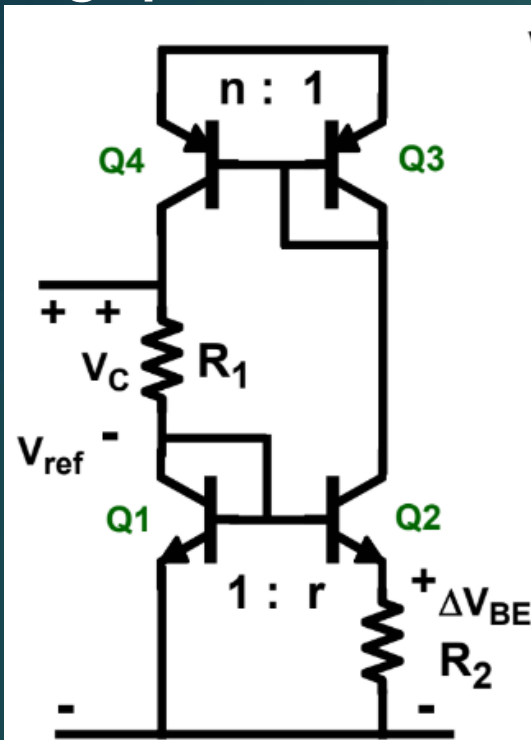

- Bandgap reference circuit provides a constant output voltage across a wide temperature range.
- The circuit consists of:
  - CTAT – a negatively proportional to absolute temperature component, in this case the base-emitter junction voltage of a BJT transistor in FA mode.
  - PTAT – a positively proportional to absolute temperature component with the same temperature coefficient, in this case the resistor.
  - Combined, the output voltage remains constant across this temperature range.

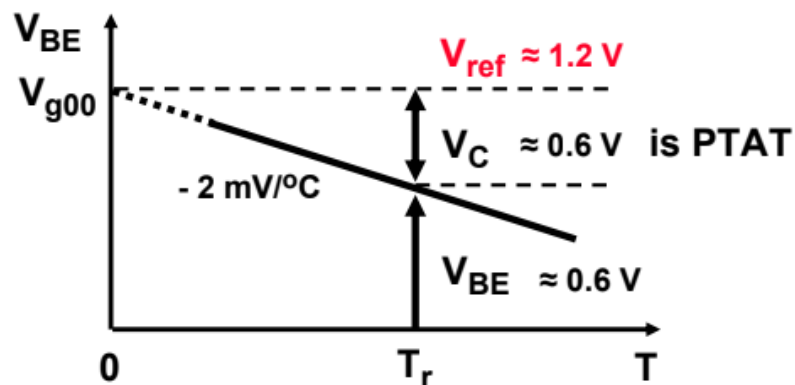

$$V_{ref} = V_{BE} + V_{R_{PTAT}} = 1.2V$$

$$I_C = CT^n \exp \left( \frac{V_{BE} - V_{g0}}{kT/q} \right)$$

$$V_{BE} = V_{g00} - \lambda T + c(T)$$

$$\Delta V_{BE} = V_{BE1} - V_{BE2} = \frac{kT}{q} \ln \frac{I_{S2}}{I_{S1}}$$

$$\Delta V_{BE} = \frac{kT}{q} \ln nr$$

$$I_{C2} = \frac{kT}{qR_2} \ln nr$$

$$V_C = n \frac{R_1}{R_2} \frac{kT}{q} \ln nr$$